

VHDL - FSM

2015.07.22


강의자 : **23기** 백두현

목차

- FSM이란?
- Moore machine
- Mealy machine
- 과제 : 신호등

FSM 이란?

□ FSM(Finite State Machine)

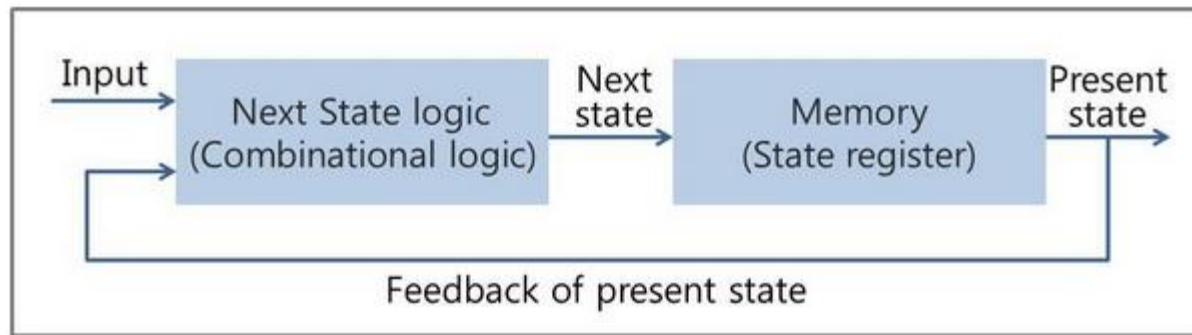

“Sequential하게 Finite한 개수의 State를 State Transition하는 Machine이다.”
(순차적으로 State 변이하는 유한한 개수의 State로 이루어진 장치.)

FSM 이란?

☐ Sequential Logic과 Combinational Logic

■ Combinational Logic(조합회로)


- ☐ Present Output은 Present Input에 관하여만 영향을 미침.

■ Sequential Logic(순차회로)

- ☐ Past Input이 계속 Present Output에 영향을 미침.
- ☐ Sequential Logic = Combinational Logic + Memory

FSM 이란?

□ State Diagram


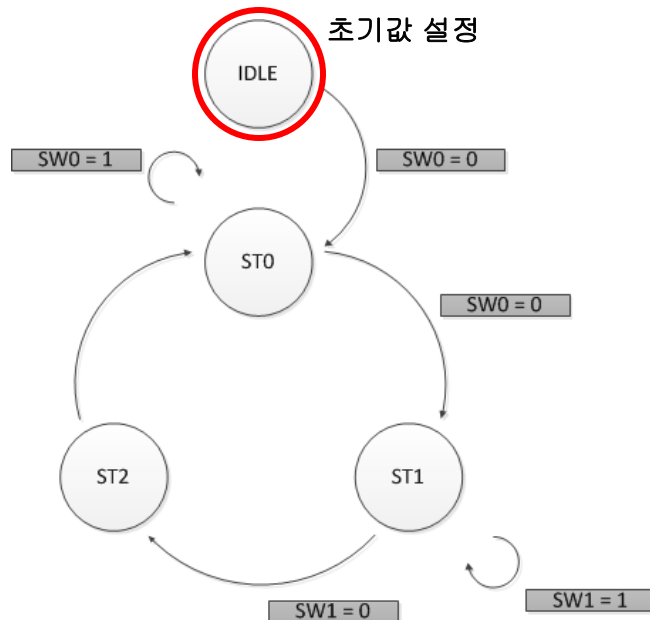


- State간의 이동을 나타낸다.
- 해당 State에서 취할 행동을 결정한다.

좋은 State Machine 일수록 State가 간결해 진다.
=> System의 소요시간이 줄어든다.

Moore Machine

 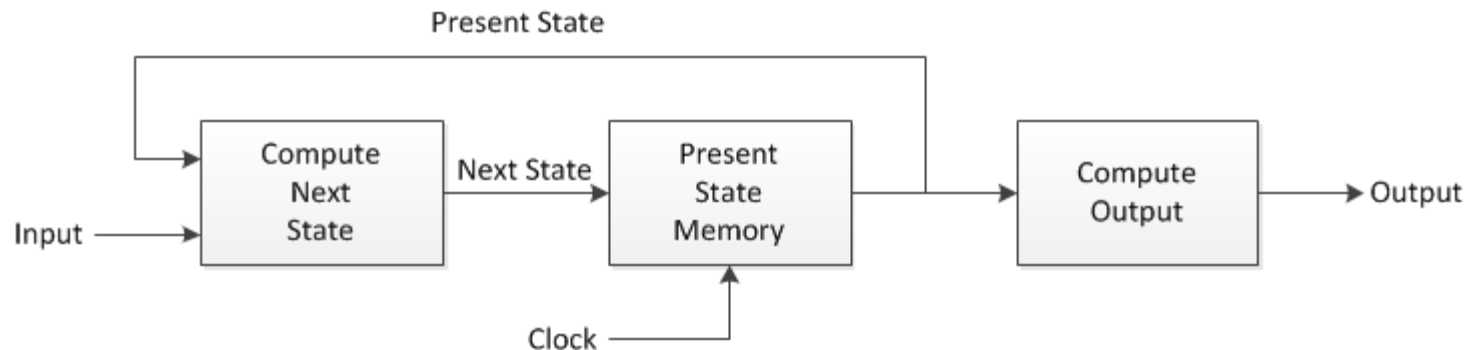- Moore Machine - Output only depends upon Present State.
 - Outputs are unconditional(not directly dependent on input signal)




GENERIC MOORE STATE MACHINE

Moore Machine

Moore Machine Source(From ALTERA)

```
1  -- A Moore machine's outputs are dependent only on the current state.
2  -- The output is written only when the state changes. (State
3  -- transitions are synchronous.)
4
5  library ieee;
6  use ieee.std_logic_1164.all;
7
8  entity moore_4s is
9
10     port(
11         clk      : in std_logic;
12         data_in   : in std_logic;
13         reset     : in std_logic;
14         data_out  : out std_logic_vector(1 downto 0)
15     );
16
17 end entity;
18
19 architecture rtl of moore_4s is
20
21     -- Build an enumerated type for the state machine
22     type state_type is (s0, s1, s2, s3);
23
24     -- Register to hold the current state
25     signal state : state_type;
26
27 begin
28     -- Logic to advance to the next state
29     process (clk, reset)
30     begin
31         if reset = '1' then
32             state <= s0;
33         elsif (rising_edge(clk)) then
34             case state is
35                 when s0 =>
36                     if data_in = '1' then
37                         state <= s1;
38                     else
39                         state <= s0;
40                     end if;
41                 when s1 =>
42                     if data_in = '1' then
43                         state <= s2;
44                     else
45                         state <= s1;
46                     end if;
47                 when s2 =>
48                     if data_in = '1' then
49                         state <= s3;
50                     else
51                         state <= s2;
52                     end if;
53                 when s3 =>
54                     if data_in = '1' then
55                         state <= s0;
56                     else
57                         state <= s3;
58                     end if;
59             end case;
60         end if;
61     end process;
```



```
62
63     -- Output depends solely on the current state
64     process (state)
65     begin
66
67         case state is
68             when s0 =>
69                 data_out <= "00";
70             when s1 =>
71                 data_out <= "01";
72             when s2 =>
73                 data_out <= "10";
74             when s3 =>
75                 data_out <= "11";
76         end case;
77     end process;
78
79 end rtl;
80
```

 

Mealy Machine

□ Mealy Machine – Outputs determined by the current state and the current inputs.

 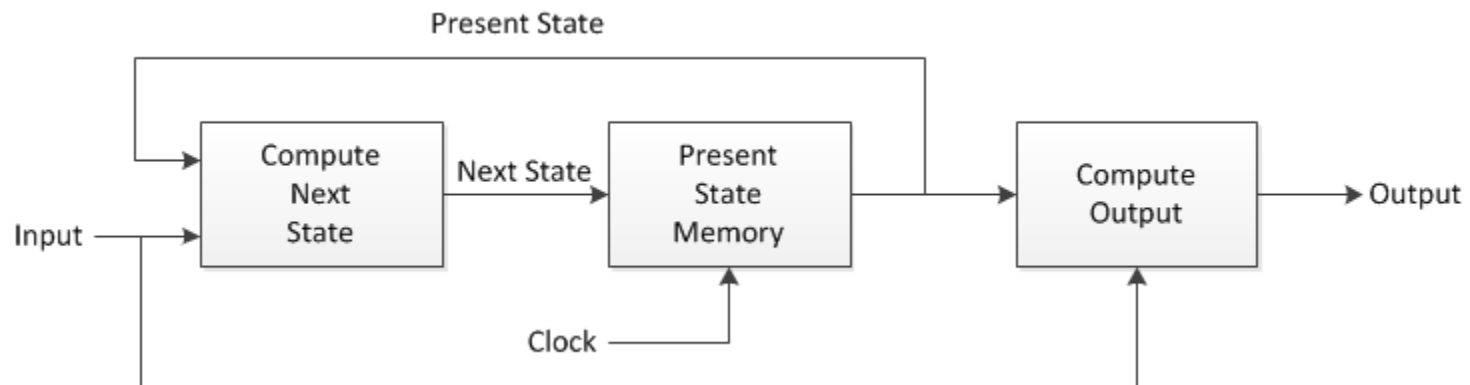- Outputs are conditional(directly dependent on input signals)




GENERIC MEALY STATE MACHINE

Mealy Machine


Mealy Machine Source(From ALTERA)

```
1  -- A Mealy machine has outputs that depend on both the state and
2  -- the inputs. When the inputs change, the outputs are updated
3  -- immediately, without waiting for a clock edge. The outputs
4  -- can be written more than once per state or per clock cycle.
5
6  library ieee;
7  use ieee.std_logic_1164.all;
8
9  entity mealy_4s is
10
11  port
12  (
13    clk      : in std_logic;
14    data_in  : in std_logic;
15    reset    : in std_logic;
16    data_out : out std_logic_vector(1 downto 0)
17  );
18
19  end entity;
20
21  architecture rtl of mealy_4s is
22
23    -- Build an enumerated type for the state machine
24    type state_type is (s0, s1, s2, s3);
25
26    -- Register to hold the current state
27    signal state : state_type;
28
29  begin
30    process (clk, reset)
31    begin
32      if reset = '1' then
33        state <= s0;
34      elsif (rising_edge(clk)) then
35        -- Determine the next state synchronously, based on
36        -- the current state and the input
37        case state is
38          when s0=>
39            if data_in = '1' then
40              state <= s1;
41            else
42              state <= s0;
43            end if;
44          when s1=>
45            if data_in = '1' then
46              state <= s2;
47            else
48              state <= s1;
49            end if;
50          when s2=>
51            if data_in = '1' then
52              state <= s3;
53            else
54              state <= s2;
55            end if;
56          when s3=>
57            if data_in = '1' then
58              state <= s3;
59            else
60              state <= s1;
61            end if;
62          end case;
63        end if;
64      end process;
65
66
```

```
67  -- Determine the output based only on the current state
68  -- and the input (do not wait for a clock edge).
69  process (state, data_in)
70  begin
71    case state is
72      when s0=>
73        if data_in = '1' then
74          data_out <= "00";
75        else
76          data_out <= "01";
77        end if;
78      when s1=>
79        if data_in = '1' then
80          data_out <= "01";
81        else
82          data_out <= "11";
83        end if;
84      when s2=>
85        if data_in = '1' then
86          data_out <= "10";
87        else
88          data_out <= "10";
89        end if;
90      when s3=>
91        if data_in = '1' then
92          data_out <= "11";
93        else
94          data_out <= "10";
95        end if;
96      end case;
97    end process;
98
99  end rtl;
100
```

 

Mealy Machine ?? Moore Machine??

 

- Mealy 또는 Moore Machine의 선택은 시스템에 맞추어 간다.
- 시스템에 따라 Mealy 와 Moore Machine 모두 쓰일 수 있다.
- State Machine의 Source는 규정 되어 있지 않다.